

LAB # 12



Fall 2020

CSE304L Computer Organization & Architecture Lab

Submitted by: **ASHLEY ALEX JACOB**

Registration No: **18PWCSE1649**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

Submitted to:

Engr. Amaad Khalil

March 18, 2021 (Thursday)

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Lab Tasks:

Task:

Write a Verilog code for Half Adder using Gate Level modeling.

Code:

```
module halfAdder( output s,c,input a,b);
```

```
and(c,a,b);
```

```
xor(s,a,b);
```

```
endmodule
```

```
module stimHaldAdd();
```

```
wire S,C;
```

```
reg A,B;
```

```
halfAdder ha(S,C,A,B);
```

```
initial
```

```
begin
```

```
$display("A      B      S      C");
```

```
A=0;
```

```
B=0;
```

```
#1 $display("%b      %b      %b      %b",A,B,S,C);
```

```
A=0;
```

```
B=1;
```

```
#1 $display("%b      %b      %b      %b",A,B,S,C);
```

```
A=1;
```

```
B=0;
```

```
#1 $display("%b      %b      %b      %b",A,B,S,C);
```


```
A=1;
```

```
B=1;
```


```
#1 $display("%b      %b      %b      %b",A,B,S,C);
```

```
end
```

endmodule

 
 
```
vsim ash.stimHaldAdd
# vsim ash.stimHaldAdd
# Loading ash.stimHaldAdd
# Loading ash.halfAdder
run
# A  B  S  C
# 0  0  0  0
# 0  1  1  0
# 1  0  1  0
# 1  1  0  1
destroy .wave
```



Task:

Write a Verilog code for Full Adder using Gate Level modeling.

Code:

```
module fullAdder( output s,cOut,input a,b,cIn);

xor(n1,a,b),(s,cIn,n1);

and(n2,n1,cIn),(n3,a,b);

or(cOut,n2,n3);
```

```
endmodule
```

```
module stimFullAdd();
```

```
wire S,Cout;
```

```
reg A,B,Cin;
```

```
fullAdder fa(S,Cout,A,B,Cin);
```

```
initial
```

```
begin
```

```
$display("Cin   A       B       S       Cout");
```

```
Cin=0;
```

```
A=0;
```

```
B=0;
```

```
#1 $display("%b       %b       %b       %b       %b",Cin,A,B,S,Cout);
```

```
Cin=0;
```

A=0;

B=1;

#1 \$display("%b %b %b %b %b",Cin,A,B,S,Cout);

Cin=0;

A=1;

B=0;

#1 \$display("%b %b %b %b %b",Cin,A,B,S,Cout);

Cin=0;

A=1;

B=1;

#1 \$display("%b %b %b %b %b",Cin,A,B,S,Cout);

Cin=1;

A=0;

B=0;

#1 \$display("%b %b %b %b %b",Cin,A,B,S,Cout);

Cin=1;

A=0;

B=1;

```
#1 $display("%b    %b    %b    %b    %b",Cin,A,B,S,Cout);
```

```
Cin=1;
```

```
A=1;
```

```
B=0;
```

```
#1 $display("%b    %b    %b    %b    %b",Cin,A,B,S,Cout);
```

```
Cin=1;
```

```
A=1;
```



```
B=1;
```

```
#1 $display("%b    %b    %b    %b    %b",Cin,A,B,S,Cout);
```

```
end
```

```
endmodule
```

```
| vsim ash.stimFullAdd  
| # vsim ash.stimFullAdd  
| # Loading ash.stimFullAdd  
| # Loading ash.fullAdder  
| run  
| # Cin  A  B  S  Cout  
| # 0  0  0  0  0  
| # 0  0  1  1  0  
| # 0  1  0  1  0  
| # 0  1  1  0  1  
| # 1  0  0  1  0  
| # 1  0  1  0  1  
| # 1  1  0  0  1  
| # 1  1  1  1  1  
| VSIM 7>
```

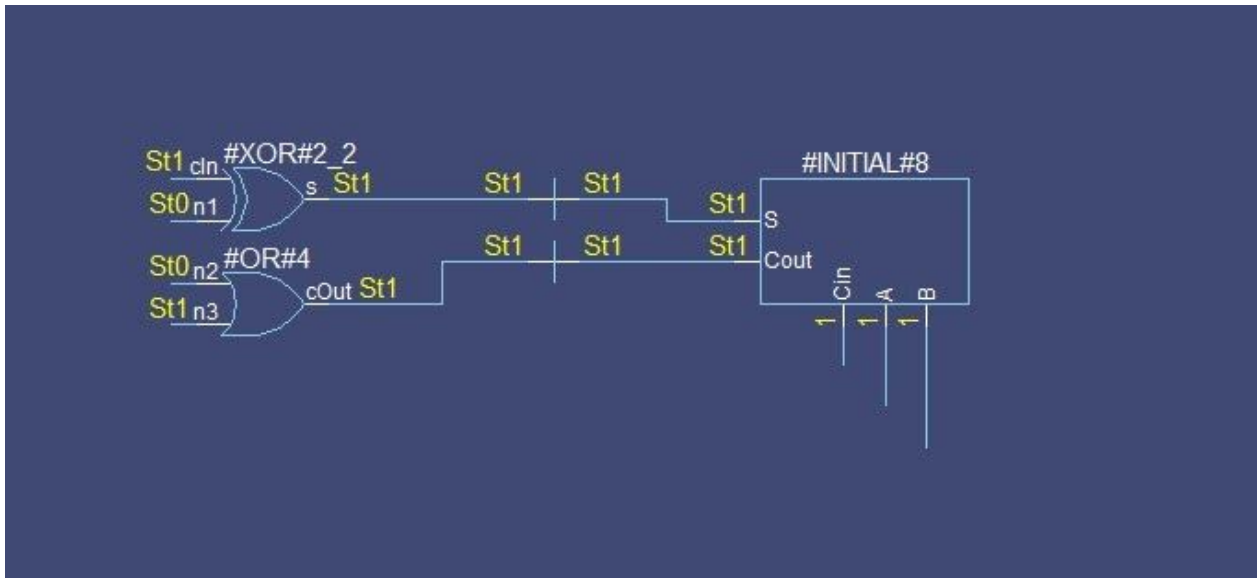 

Task:

Write a Verilog code for Half Subtractor using Gate Level modeling.

Code:

```
module halfSubtractor(output d,bo,input a,b);

xor(d,a,b);

not(a_,a);

and(bo,a_);
```



```
endmodule
```

```
module stimHSub();
```

```
  wire D,Bo;
```

```
  reg A,B;
```

```
  halfSubtractor hs(D,Bo,A,B);
```

```
  initial
```

```
  begin
```

```
    $display("A      B      D      B");
```

```
    A=0;
```

```
    B=0;
```

```
    #1 $display("%b      %b      %b      %b",A,B,D,Bo);
```

```

A=0;

B=1;

#1 $display("%b      %b      %b      %b",A,B,D,Bo);

A=1;

B=0;

#1 $display("%b      %b      %b      %b",A,B,D,Bo);

A=1;


B=1;

#1 $display("%b      %b      %b      %b",A,B,D,Bo);

end

endmodule

```

 

```

/SIM ash.stimHSub
# vsim ash.stimHSub
# Loading ash.stimHSub
# Loading ash.halfSubtractor
un
#A B D B
#0 0 0 1
#0 1 1 1
#1 0 1 0
#1 1 0 0

/SIM 33>

```

