 


University of Engineering & Technology, Peshawar
DEPARTMENT OF COMPUTER SYSTEM ENGINEERING
Fall 2021



LAB 10 part 2
Muxes,Adder,Subrtracter
(CSE-304L)


Computer Organization and Architecture Lab
Submitted By: Anis Ahmad
Reg NO: 19PWCSE1770
Submitted to: Dr. Ammad Khalil

TASK01: Muxes

Write a Verilog code for 2x1, 4x1 and 8x1 multiplexer using Gate Level modeling.

a) 2x1

Code:

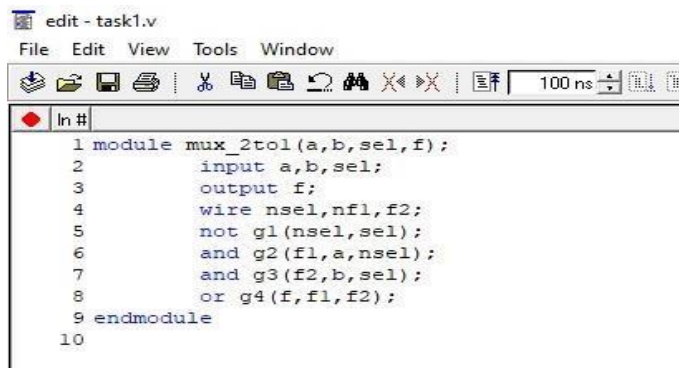

```
edit - task1.v
File Edit View Tools Window
100 ns
In #
1 module mux_2to1(a,b,sel,f);
2     input a,b,sel;
3     output f;
4     wire nsel,nf1,f2;
5     not g1(nsel,sel);
6     and g2(f1,a,nsel);
7     and g3(f2,b,sel);
8     or g4(f,f1,f2);
9 endmodule
10
```


edit - task1b.v

File Edit View Tools Window



```
1
2 module stimN();
3     reg a,b,sel;
4     wire f;
5     mux_2to1 M(a,b,sel,f);
6     initial
7     begin
8         $display("A B SEL F");
9         a=0;
10        b=0;
11        sel=0;
12        #1 $display("%b %b %b %b",a,b,sel,f);
13        #5 a=0;
14        b=0;
15        sel=1;
16        $display("%b %b %b %b",a,b,sel,f);
17        #5 a=0;
18        b=1;
19        sel=0;
20        $display("%b %b %b %b",a,b,sel,f);
21        #5 a=0;
22        b=1;
23        sel=1;
24        $display("%b %b %b %b",a,b,sel,f);
25        #5 a=1;
26        b=0;
27        sel=0;
28        $display("%b %b %b %b",a,b,sel,f);
29        #5 a=1;
30        b=0;
31        sel=1;
32        $display("%b %b %b %b",a,b,sel,f);
33        #5 a=1;
34        b=1;
35        sel=0;
36        $display("%b %b %b %b",a,b,sel,f);
37        #5 a=1;
38        b=1;
39        sel=1;
40        $display("%b %b %b %b",a,b,sel,f);
41    end
42 endmodule
```

Output Wave:

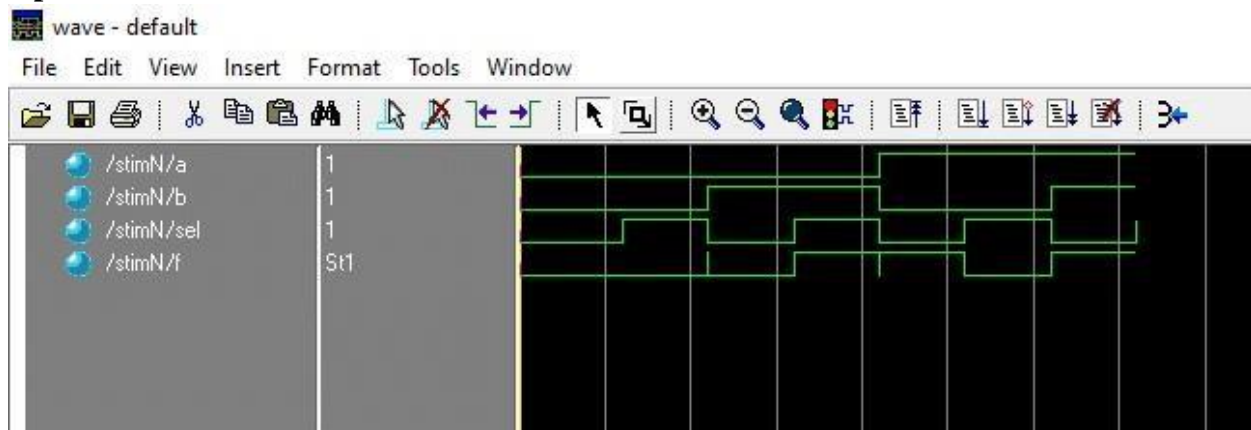

b) 4x1

Code:

```
1  
2 module mux_4to1(s1,s2,d0,d1,d2,d3,f);  
3     input s1,s2,d0,d1,d2,d3;  
4     output f;  
5     wire ns1,ns2,a0,a1,a2,a3,aa0,aa1,aa2,aa3,on1,on2;  
6     not n1(ns1,s1);  
7     not n2(ns2,s2);  
8     and g1(a0,ns1,ns2);  
9     and g11(aa0,a0,d0);  
10    and g2(a1,ns1,s2);  
11    and g22(aa1,a1,d1);  
12    and g3(a2,s1,ns2);  
13    and g33(aa2,a2,d2);  
14    and g4(a3,s1,s2);  
15    and g44(aa3,a3,d3);  
16    or o1(on1,aa0,aa1);  
17    or o2(on2,aa2,aa3);  
18    or o3(f,on1,on2);  
19 endmodule
```

```

module stim_mux4to1();
reg s1,s2,d0,d1,d2,d3;
wire f;
mux_4to1 multi(s1,s2,d0,d1,d2,d3,f); initial
begin
    $display("SEL1 SEL2 D0 D1 D2 D3");

    s1=0; s2=0; d0=0;d1=0;d2=0;d3=0;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0; d0 = 0; d1 = 0; d2 = 0; d3 = 1;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
    s1 = 0;          s2 = 0;d0 = 0; d1 = 0; d2 = 1; d3 = 0;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0; d0 = 0; d1 = 0; d2 = 1; d3 = 1;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0; d0 = 0; d1 = 1; d2 = 0; d3 = 0;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0; d0 = 0; d1 = 1; d2 = 0; d3 = 1;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
    s1 = 0;          s2 = 0; d0 = 0; d1 = 1; d2 = 1; d3 = 1;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0; s2 = 0; d0 = 1; d1 = 0; d2 = 0; d3 = 0;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
    s1 = 0; s2 = 0; d0 = 1; d1 = 0; d2 = 0; d3 = 1;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0; d0 = 1; d1 = 0; d2 = 1; d3 = 0;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0; d0 = 1; d1 = 0; d2 = 1; d3 = 1;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0;
    d0 = 1; d1 = 1; d2 = 0; d3 = 0;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
    s1 = 0;          s2 = 0;
    d0 = 1; d1 = 1; d2 = 0; d3 = 1;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0; d0 = 1; d1 = 1; d2 = 1; d3 = 0;
    #10 $display("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 0; d0 = 1; d1 = 1; d2 = 1; d3 = 1;
    #10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

    s1 = 0;          s2 = 1;d0 = 0; d1 = 0; d2 = 0; d3 = 0;

```

```

#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0; s2 = 1; d0 = 0; d1 = 0; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0; s2 = 1; d0 = 0; d1 = 0; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1; d0 = 0; d1 = 0; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1;
d0 = 0; d1 = 1; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1;
d0 = 0; d1 = 1; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1; d0 = 0; d1 = 1; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1; d0 = 1; d1 = 0; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1; d0 = 1; d1 = 0; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1; d0 = 1; d1 = 0; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 0;          s2 = 1; d0 = 1; d1 = 0; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0; s2 = 1; d0 = 1; d1 = 1; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 0;          s2 = 1; d0 = 1; d1 = 1; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1;
d0 = 1; d1 = 1; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 0;          s2 = 1;
d0 = 1; d1 = 1; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 0; d1 = 0; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;

```

```

d0 = 0; d1 = 0; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 0; d1 = 0; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 0; d1 = 0; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 0; d1 = 1; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 1; s2 = 0; d0 = 0; d1 = 1; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 1; s2 = 0; d0 = 0; d1 = 1; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 1;          s2 = 0;
d0 = 1; d1 = 0; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 1; d1 = 0; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 1; d1 = 0; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 1; d1 = 0; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 1; d1 = 1; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0;
d0 = 1; d1 = 1; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 0; d0 = 1; d1 = 1; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 1; s2 = 0; d0 = 1; d1 = 1; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 1; s2 = 0; d0 = 0; d1 = 0; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1;

```

```

d0 = 0; d1 = 0; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1; d0 = 0; d1 = 0; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1; d0 = 0; d1 = 0; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1;          d0 = 0; d1 = 1; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1; d0 = 0; d1 = 1; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1; d0 = 0; d1 = 1; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1; d0 = 1; d1 = 0; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1; s2 = 1; d0 = 1; d1 = 0; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 1; s2 = 1; d0 = 1; d1 = 0; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1; d0 = 1; d1 = 0; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
s1 = 1;          s2 = 1; d0 = 1; d1 = 1; d2 = 0; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);


s1 = 1;          s2 = 1; d0 = 1; d1 = 1; d2 = 0; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1; d0 = 1; d1 = 1; d2 = 1; d3 = 0;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);

s1 = 1;          s2 = 1; d0 = 1; d1 = 1; d2 = 1; d3 = 1;
#10 $ display ("%b %b %b %b %b %b %b",s1,s2,d0,d1,d2,d3,f);
end
endmodule

```

Output Wave:

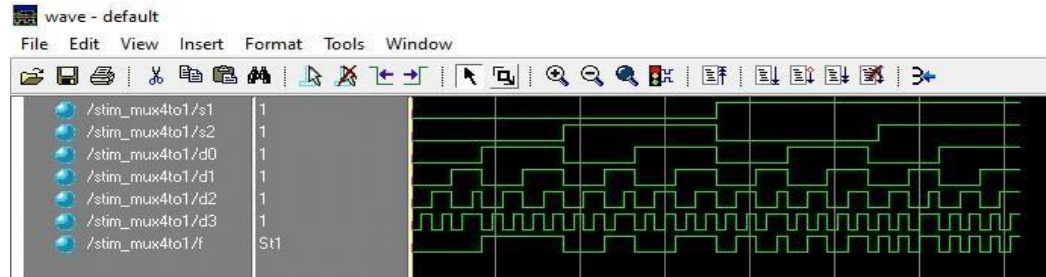

c) 8x1

Code:

```

edit - mux8to1a.v
File Edit View Tools Window
100 ns
In # E
1
2 module mux_8to1(s1,s2,s3,in0,in1,in2,in3,in4,in5,in6,in7,f);
3     input s1,s2,s3,in0,in1,in2,in3,in4,in5,in6,in7;
4     output f;
5     wire ns1,ns2,ns3,a0,a1,a2,a3,a4,a5,a6,a7;
6     not n1(ns1,s1);
7     not n2(ns2,s2);
8     not n3(ns3,s3);
9     and g0(a0,ns1,ns2,ns3,in0);
10    and g1(a1,s1,ns2,ns3,in1);
11    and g2(a2,ns1,s2,ns3,in2);
12    and g3(a3,s1,s2,ns3,in3);
13    and g4(a4,ns1,ns2,s3,in4);
14    and g5(a5,s1,ns2,s3,in5);
15    and g6(a6,ns1,s2,s3,in6);
16    and g7(a7,s1,s2,s3,in7);
17    or o1(f,a0,a1,a2,a3,a4,a5,a6,a7);
18 endmodule

```

```

1
2 module stim_Stol;
3     reg s1,s2,s3,in0,in1,in2,in3,in4,in5,in6,in7;
4     wire f;
5     mux_Stol multipl(s1,s2,s3,in0,in1,in2,in3,in4,in5,in6,in7,f);
6     initial
7     begin
8
9         $display("SEL3 SEL2 SEL1 IN7 IN6 IN5 IN4 IN3 IN2 IN1 IN0 F");
10        s1 = 0; s2 = 0; s3 = 0;
11        in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
12        #1 $display("%b %b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
13        #5;
14
15        s1 = 0; s2 = 0; s3 = 0;
16        in0=1;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
17        #1 $display("%b %b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
18        #5;
19
20        s1 = 1; s2 = 0; s3 = 0;
21        in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
22        #1 $display("%b %b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
23        #5;
24
25        s1 = 1; s2 = 0; s3 = 0;
26        in0=0;in1=1;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
27        #1 $display("%b %b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
28        #5;
29
30        s1 = 0; s2 = 1; s3 = 0;
31        in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
32        #1 $display("%b %b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
33        #5;
34
35        s1 = 0; s2 = 1; s3 = 0;
36        in0=0;in1=0;in2=1;in3=0;in4=0;in5=0;in6=0;in7=0;
37        #1 $display("%b %b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
38        #5;
39
40        s1 = 1; s2 = 1; s3 = 0;
41        in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
42        #1 $display("%b %b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
43        #5;
44
45
46
47
48
49
50
51
52
53
54
55
56
57
58
59
60
61
62
63
64
65
66
67
68
69
70
71
72
73
74
75
76
77
78
79
80
81
82
83
84
85
86
87
88
89
90
91
92
93
94
95
96
97
98
99


```

```

44     s1 = 1; s2 = 1; s3 = 0;
45     in0=0;in1=0;in2=0;in3=1;in4=0;in5=0;in6=0;in7=0;
46     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
47     #5;
48
49     s1 = 0; s2 = 0; s3 = 1;
50     in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
51     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
52     #5;
53
54     s1 = 0; s2 = 0; s3 = 1;
55     in0=0;in1=0;in2=0;in3=0;in4=1;in5=0;in6=0;in7=0;
56     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
57     #5;
58
59     s1 = 1; s2 = 0; s3 = 1;
60     in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
61     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
62     #5;
63
64     s1 = 1; s2 = 0; s3 = 1;
65     in0=0;in1=0;in2=0;in3=0;in4=0;in5=1;in6=0;in7=0;
66     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
67     #5;
68
69     s1 = 0; s2 = 1; s3 = 1;
70     in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
71     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
72     #5;
73
74     s1 = 0; s2 = 1; s3 = 1;
75     in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=1;in7=0;
76     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
77     #5;
78
79     s1 = 1; s2 = 1; s3 = 1;
80     in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=0;
81     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
82     #5;
83     s1 = 1; s2 = 1; s3 = 1;
84     in0=0;in1=0;in2=0;in3=0;in4=0;in5=0;in6=0;in7=1;
85     #1 $display("%b %b %b %b %b %b %b %b %b %b",s3,s2,s1,in7,in6,in5,in4,in3,in2,in1,in0,f);
86     #5;
87     end
88 endmodule

```


Output Wave:

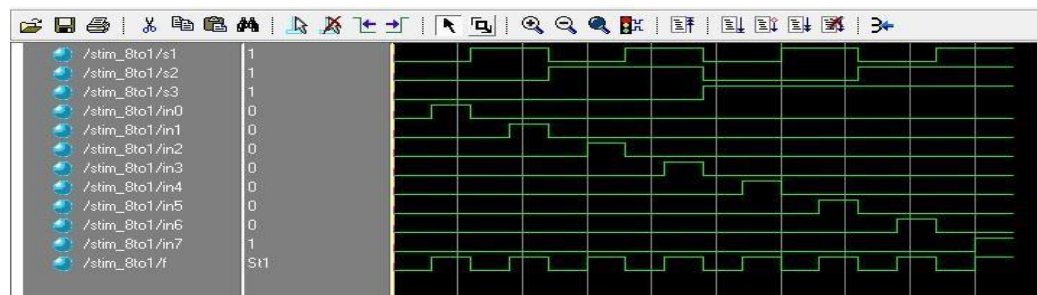

TASK01:

Write a Verilog code for Half Adder using Gate Level modeling


Code:

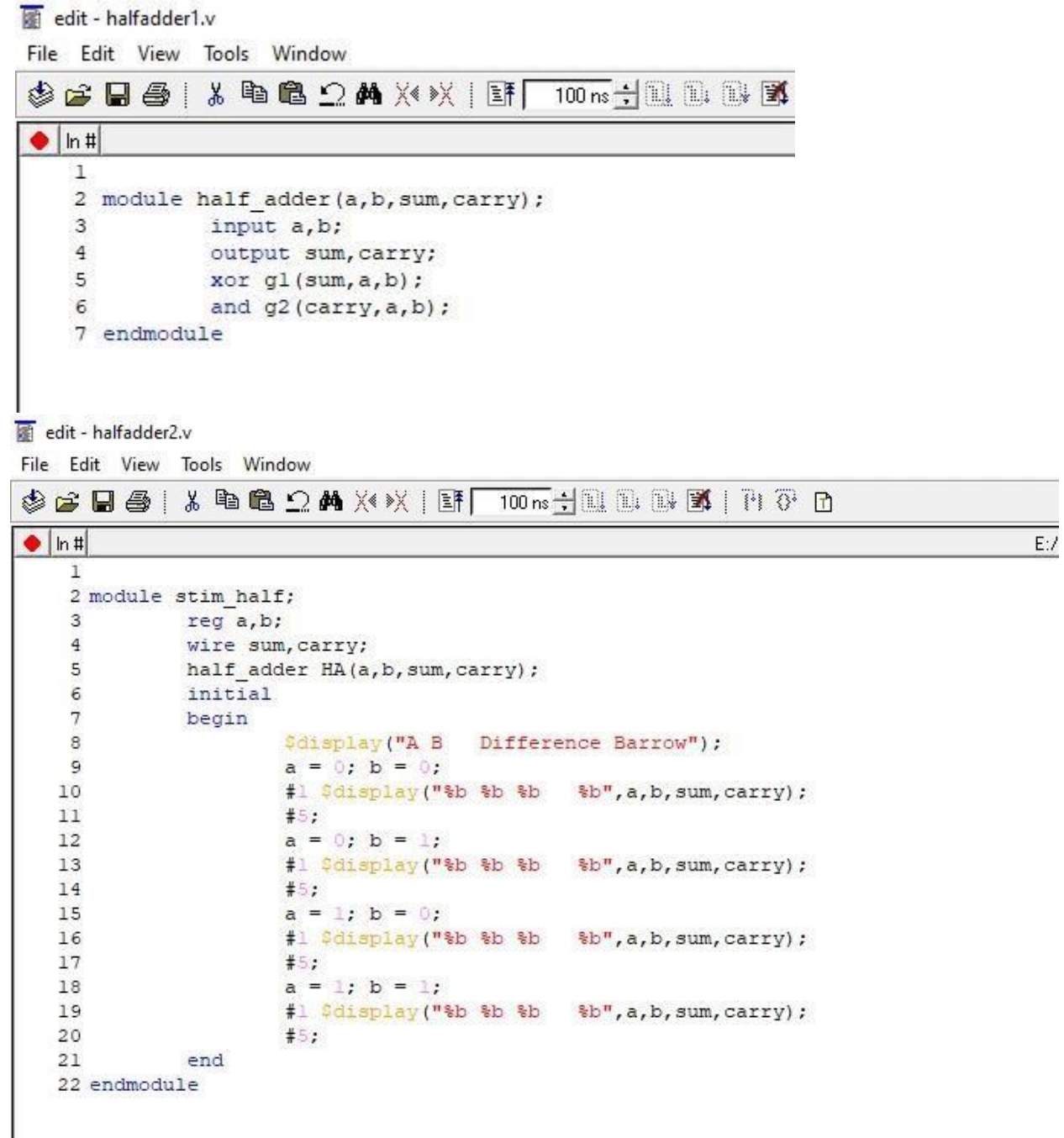

```
edit - halfadder1.v
File Edit View Tools Window
100 ns
In #
1
2 module half_adder(a,b,sum,carry);
3     input a,b;
4     output sum,carry;
5     xor g1(sum,a,b);
6     and g2(carry,a,b);
7 endmodule

edit - halfadder2.v
File Edit View Tools Window
100 ns
In # E:/
1
2 module stim_half;
3     reg a,b;
4     wire sum,carry;
5     half_adder HA(a,b,sum,carry);
6     initial
7     begin
8         $display("A B Difference Barrow");
9         a = 0; b = 0;
10        #1 $display("%b %b %b %b",a,b,sum,carry);
11        #5;
12        a = 0; b = 1;
13        #1 $display("%b %b %b %b",a,b,sum,carry);
14        #5;
15        a = 1; b = 0;
16        #1 $display("%b %b %b %b",a,b,sum,carry);
17        #5;
18        a = 1; b = 1;
19        #1 $display("%b %b %b %b",a,b,sum,carry);
20        #5;
21    end
22 endmodule
```

Output Wave:

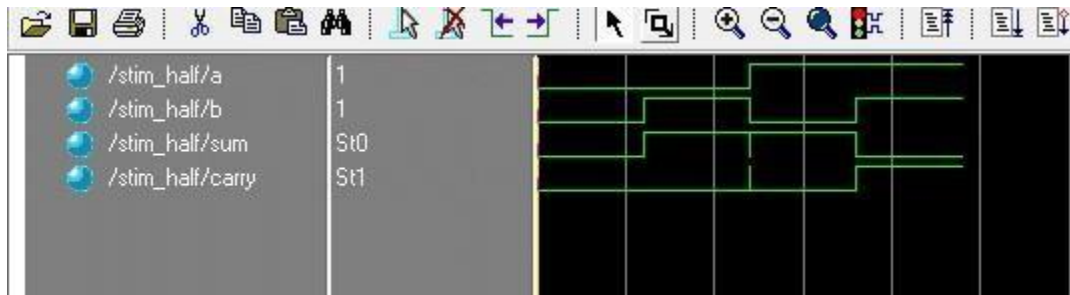

TASK02:

Write a Verilog code for Full Adder using Gate Level modeling.

Code:

```
edit - Fulladder1.v
File Edit View Tools Window
100 ns
Ln #
1
2 module full_adder(a,b,c,sum,carry);
3     input a,b,c;
4     output sum,carry;
5     wire a1,a2,a3;
6
7     xor g1(sum,a,b,c);
8     xor g2(a1,a,b);
9     and g3(a2,a,b);
10    and g4(a3,a1,c);
11    or g5(carry,a2,a3);
12 endmodule
```


edit - Fulladder2.v
File Edit View Tools Window
100 ns

Ln #

E:/5TH SE

```

1
2 module stim_fulladd;
3     reg a,b,c;
4     wire sum,carry;
5     full_adder fulad(a,b,c,sum,carry);
6     initial
7     begin
8         $display("A B   Cin   Sum   carry");
9         a = 0; b = 0; c = 0;
10        #1 $display("%b %b %b   %b   %b",a,b,c,sum,carry);
11        #5;
12        a = 0; b = 0; c = 1;
13        #1 $display("%b %b %b   %b   %b",a,b,c,sum,carry);
14        #5;
15        a = 0; b = 1; c = 0;
16        #1 $display("%b %b %b   %b   %b",a,b,c,sum,carry);
17        #5;
18        a = 0; b = 1; c = 1;
19        #1 $display("%b %b %b   %b   %b",a,b,c,sum,carry);
20        #5;
21        a = 1; b = 0; c = 0;
22        #1 $display("%b %b %b   %b   %b",a,b,c,sum,carry);
23        #5;
24        a = 1; b = 0; c = 1;
25        #1 $display("%b %b %b   %b   %b",a,b,c,sum,carry);
26        #5;
27        a = 1; b = 1; c = 0;
28        #1 $display("%b %b %b   %b   %b",a,b,c,sum,carry);
29        #5;
30        a = 1; b = 1; c = 1;
31        #1 $display("%b %b %b   %b   %b",a,b,c,sum,carry);
32        #5;
33    end
34 endmodule

```

Output Wave:

wave - default
File Edit View Insert Format Tools Window

/stim_fulladd/a
/stim_fulladd/b
/stim_fulladd/c
/stim_fulladd/sum
/stim_fulladd/carry

1
1
1
S1
S1

TASK03:

Write a Verilog code for Half Subtractor using Gate Level modeling.

Code:

```
1
2 module half_sub(a,b,sum,carry);
3     input a,b;
4     output sum,carry;
5     wire na;
6     not n1(na,a);
7     xor g1(sum,a,b);
8     and g2(carry,na,b);
9 endmodule
10
```

```
1
2 module stim_halfsub;
3     reg a,b;
4     wire sum,carry;
5     half_sub HS(a,b,sum,carry);
6     initial
7     begin
8         $display("A B    SUM    Carry");
9         a = 0; b = 0;
10        #1 $display("%b %b %b    %b",a,b,sum,carry);
11        #5;
12        a = 0; b = 1;
13        #1 $display("%b %b %b    %b",a,b,sum,carry);
14        #5;
15        a = 1; b = 0;
16        #1 $display("%b %b %b    %b",a,b,sum,carry);
17        #5;
18        a = 1; b = 1;
19        #1 $display("%b %b %b    %b",a,b,sum,carry);
20        #5;
21    end
22 endmodule
23
24
```

Output Wave:

