

LAB # 13



Fall 2020

CSE304L Computer Organization & Architecture Lab

Submitted by: **ASHLEY ALEX JACOB**

Registration No: **18PWCSE1649**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

Submitted to:

Engr. Amaad Khalil

March 19, 2021 (Friday)

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Lab Tasks:

Task:

Write a Verilog code for 2x1 MUX using Dataflow Level modeling.

Code:

```
module mux2x1(output o,input a,b,s);
```

```
    wire as = a&s;
```

```
    wire s_= ~s;
```

```
    wire bs = b&s_;
```

```
    assign o = as | bs;
```

```
endmodule
```

```
module stimMux2x1();
```

```
    wire O;
```

```
    reg I1,I2,S;
```

```
    mux2x1 m(O,I1,I2,S);
```

```
initial
```

```
begin
```

```

$display("S      I1      I2      Y");

I1 = 0;

I2 = 0;

S = 0;

#1 $display("%b      %b      %b      %b",S,I1,I2,0);

I1 = 0;

I2 = 1;

S = 0;

#1 $display("%b      %b      %b      %b",S,I1,I2,0);

I1 = 1;

I2 = 0;

S = 1;

#1 $display("%b      %b      %b      %b",S,I1,I2,0);

I1 = 1;

I2 = 1;


S = 1;

#1 $display("%b      %b      %b      %b",S,I1,I2,0);


end

```

endmodule

 
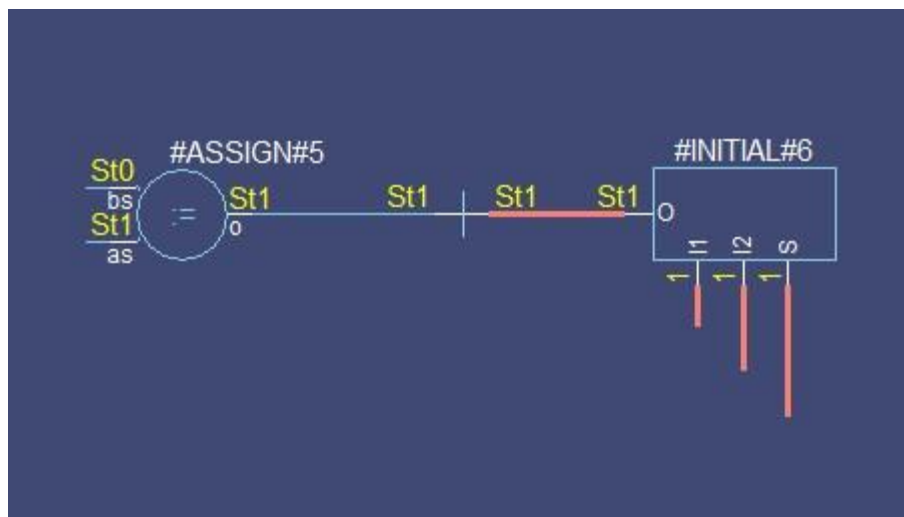
```
# Loading ash.stimMux2x1
# Loading ash.mux2x1
run
# S  I1  I2  Y
# 0  0   0   0
# 0  0   1   1
# 1  1   0   1
# 1  1   1   1
VSIM 38>
```



Task:

Write a Verilog code for 2x4 Decoder using Dataflow Level modeling.

Code:

```
module dec2x4(input a1,a0,e,output y3,y2,y1,y0);
```

```

wire na0 = ~a0;

wire na1 = ~a1;

assign y3 = a1&a0&e;

assign y2 = a1&na0&e;

assign y1 = na1&a0&e;

assign y0 = na1&na0&e;

endmodule

```

```

module stimDec2x4();

reg A0,A1,E;

wire Y3,Y2,Y1,Y0;

dec2x4 d(A1,A0,E,Y3,Y2,Y1,Y0);

initial

begin

$display("E      A1 A0      Y3 Y2 Y1 Y0");

E=0;

```

A1=1;

A0=0;

#1 \$display("%b %b %b %b %b %b"
%b",E,A1,A0,Y3,Y2,Y1,Y0);

E=1;

A1=0;

A0=0;

#1 \$display("%b %b %b %b %b %b"
%b",E,A1,A0,Y3,Y2,Y1,Y0);

E=1;

A1=0;

A0=1;

#1 \$display("%b %b %b %b %b %b"
%b",E,A1,A0,Y3,Y2,Y1,Y0);

E=1;

A1=1;

A0=0;

#1 \$display("%b %b %b %b %b %b"
%b",E,A1,A0,Y3,Y2,Y1,Y0);

E=1;

A1=1;

```
#1 $display("%b          %b          %b          %b          %b          %b\n",E,A1,A0,Y3,Y2,Y1,Y0);
```


end


endmodule

```

vsim ash.stimDec2x4
# vsim ash.stimDec2x4
# Loading ash.stimDec2x4
# Loading ash.dec2x4
run
# E  A1 A0  Y3 Y2 Y1 Y0
# 0 1 0  0 0 0 0 0
# 1 0 0  0 0 0 1
# 1 0 1  0 0 1 0
# 1 1 0  0 1 0 0
# 1 1 1  1 0 0 0
VSIM 10>

```

 

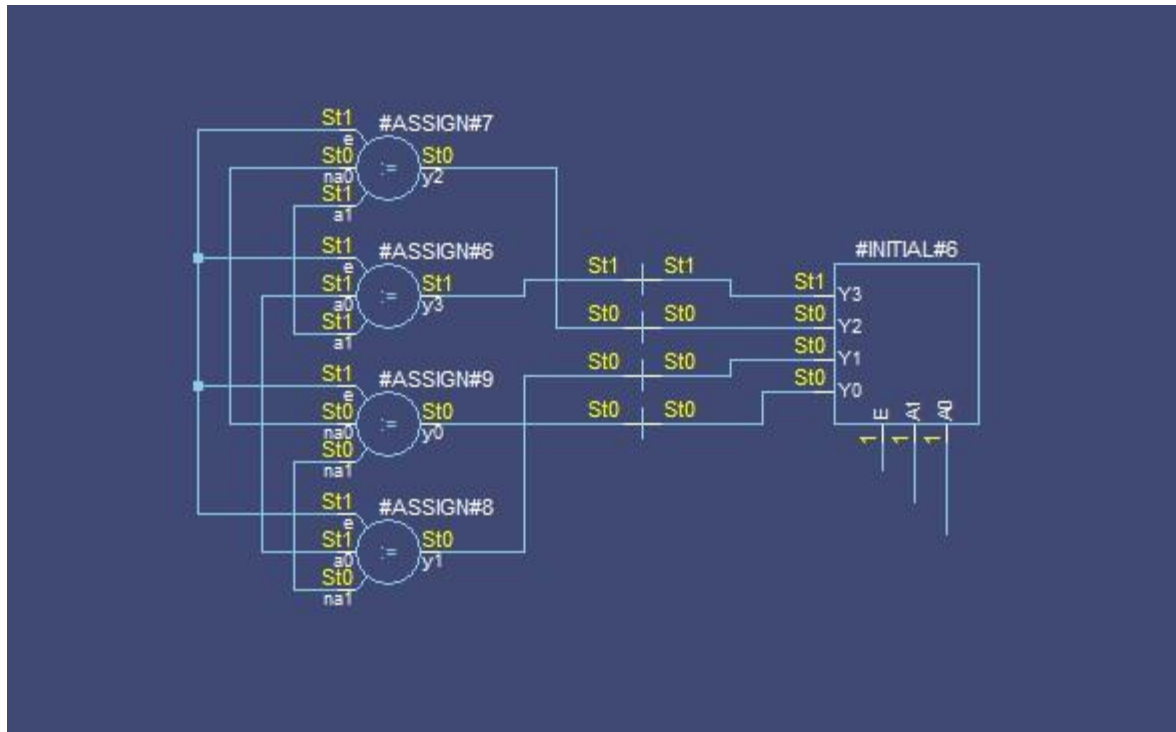

Task:

Write a Verilog code for Half Adder using Dataflow Level modeling.

Code:

```
module halfAdd(output s,c,input a,b);
```

```
    assign c = a&b;
```

```
    assign s = a ^ b;
```

```
endmodule
```

```
module simHalfAdd();
```

```
    wire S,C;
```

```
    reg A,B;
```



```
halfAdd ha(S,C,A,B);
```

```
initial
```

```
begin
```

```
$display("A      B      S      C");
```

```
A=0;
```

```
B=0;
```

```
#1 $display("%b      %b      %b      %b",A,B,S,C);
```

```
A=0;
```

```
B=1;
```

```
#1 $display("%b      %b      %b      %b",A,B,S,C);
```

```
A=1;
```

```
B=0;
```

```
#1 $display("%b      %b      %b      %b",A,B,S,C);
```


```
A=1;
```

```
B=1;
```

```
#1 $display("%b      %b      %b      %b",A,B,S,C);
```


```
end
```

```
endmodule
```

 

```
vsim ash.simHalfAdd
# vsim ash.simHalfAdd
# Loading ash.simHalfAdd
# Loading ash.halfAdd
run
#A  B  S  C
#0  0  0  0
#0  1  1  0
#1  0  1  0
#1  1  0  1
destroy .wave
```

```
VSIM 14>
```

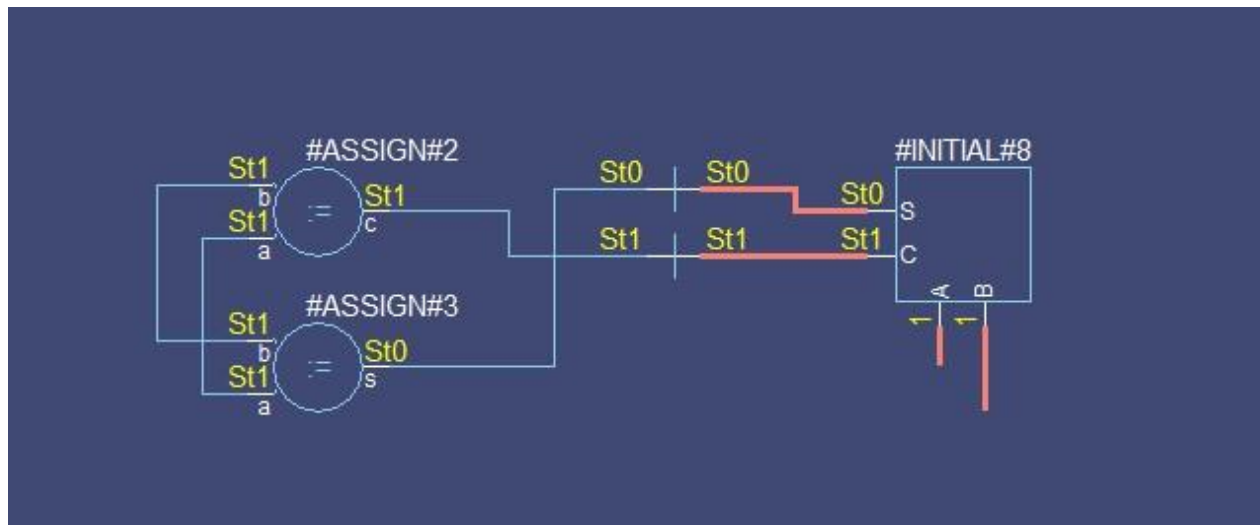

Task:

Write a Verilog code for Full Adder using Dataflow Level modeling.

Code:

```
module fullAdd( output s,cOut,input a,b,cIn);
```

```
  wire n1 = a ^ b;
```

```
  assign s = cIn ^ n1;
```

```
  wire n2 = n1 & cIn;
```

```
  wire n3 = a & b;
```

```
  assign cOut = n2 | n3;
```

```
endmodule
```

```
module simFullAdd();
```

```
wire S,Cout;
```

```
reg A,B,Cin;
```

```
fullAdd fa(S,Cout,A,B,Cin);
```

```
initial
```

```
begin
```

```
$display("Cin    A      B      S      Cout");
```

```
Cin=0;
```

```
A=0;
```

```
B=0;
```

```
#1 $display("%b    %b    %b    %b    %b",Cin,A,B,S,Cout);
```

```
Cin=0;
```

```
A=0;
```

```
B=1;
```

```
#1 $display("%b    %b    %b    %b    %b",Cin,A,B,S,Cout);
```

```
Cin=0;
```

A=1;

B=0;

#1 \$display("%b %b %b %b %b",Cin,A,B,S,Cout);

Cin=0;

A=1;

B=1;

#1 \$display("%b %b %b %b %b",Cin,A,B,S,Cout);

Cin=1;

A=0;

B=0;

#1 \$display("%b %b %b %b %b",Cin,A,B,S,Cout);

Cin=1;

A=0;

B=1;

#1 \$display("%b %b %b %b %b",Cin,A,B,S,Cout);

Cin=1;

A=1;

B=0;

```
#1 $display("%b      %b      %b      %b      %b",Cin,A,B,S,Cout);
```

```
Cin=1;
```

```
A=1;
```

```
B=1;
```


```
#1 $display("%b      %b      %b      %b      %b",Cin,A,B,S,Cout);
```


```
end
```

```
endmodule
```

```
# vsim ash.simFullAdd
# Loading ash.simFullAdd
# Loading ash.fullAdd
run
# Cin  A  B  S  Cout
#0  0  0  0  0
#0  0  1  1  0
#0  1  0  1  0
#0  1  1  0  1
#1  0  0  1  0
#1  0  1  0  1
#1  1  0  0  1
#1  1  1  1  1
```

```
VSIM 19>
```

 

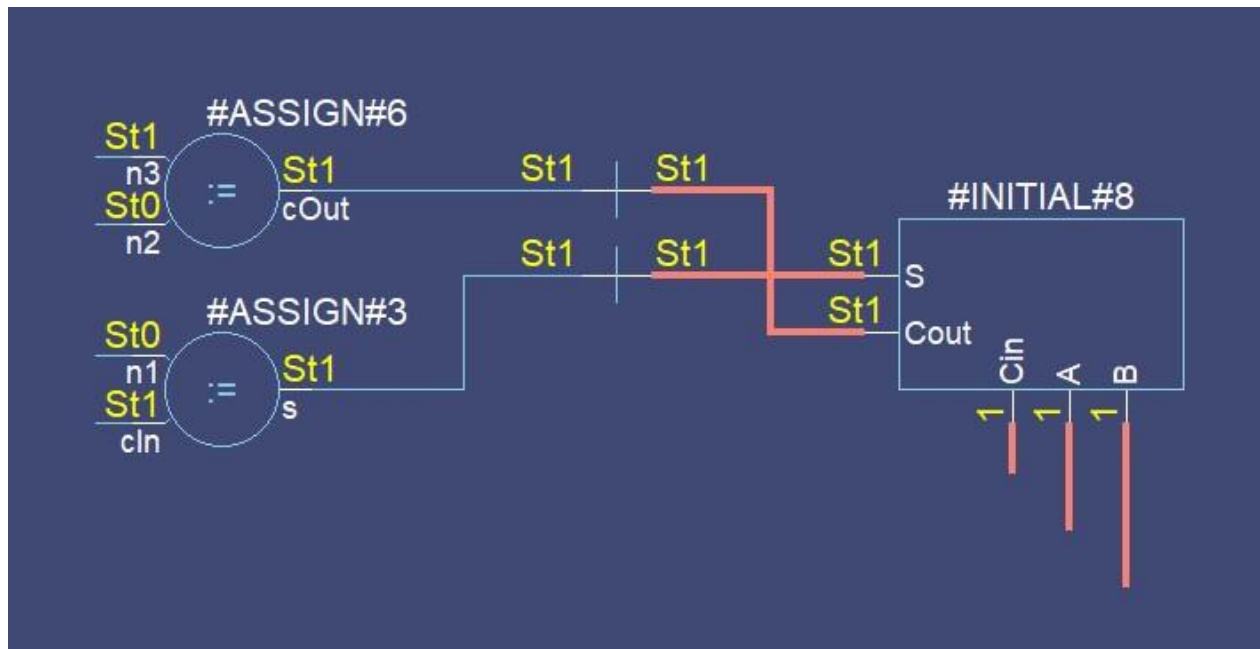

Task:

Write a Verilog code for Half Subtractor using Dataflow Level modeling.

Code:

```
module halfSub(output d,bo,input a,b);
```

```
    assign d = a ^ b;
```

```
    assign bo = b & (~a);
```

```
endmodule
```

```
module simHalfSub();
```

```
    wire D,Bo;
```

```
    reg A,B;
```

```
halfSub hs(D,Bo,A,B);
```

```
initial
```

```
begin
```

```
$display("A      B      D      B");
```

```
A=0;
```

```
B=0;
```

```
#1 $display("%b      %b      %b      %b",A,B,D,Bo);
```

```
A=0;
```

```
B=1;
```

```
#1 $display("%b      %b      %b      %b",A,B,D,Bo);
```

```
A=1;
```

```
B=0;
```

```
#1 $display("%b      %b      %b      %b",A,B,D,Bo);
```



```
A=1;
```

```
B=1;
```

```
#1 $display("%b      %b      %b      %b",A,B,D,Bo);
```

```
end
```

```
endmodule
```

```
# vsim ash.simHalfSub
# Loading ash.simHalfSub
# Loading ash.halfSub
run
#A  B  D  B
#0  0  0  0
#0  1  1  1
#1  0  1  0
#1  1  0  0
```

```
VSIM 16>
```

